

Homework 2 – Homework

Name: _____

Section: ☐ M1 ☐ T1

Homework Assignment: Submit via gradescope

1. In this problem, you will build a VHDL entity called **scancode decoder** which processes keyboard scancodes. When you press a key on a keyboard, the keyboard sends an 8-bit code to the computer called a PS2 scancode. Each key has its own scancode listed below. The relationship between the keys and their scancode is not based on ASCII nor any other discernible pattern.

Keyboard Key	0	1	2	3	4	5	6	7	8	9
Scancode (in hex)	0x45	0x16	0x1E	0x26	0x25	0x2E	0x36	0x3D	0x3E	0x46


Build a component which converts an 8-bit scancode for the digits 0-9 into a 4-bit hexadecimal values.

Nomenclature:	Scancode decoder
Data Input:	D = std_logic_vector(7 downto 0);
Data Output:	H = std_logic_vector(3 downto 0);
Control:	none
Status:	none
Behavior:	Converts the scancode D, representing a keypress of a decimal digit, into its 4-bit value. For example, if $D = 25_{16}$, the scancode for the character "4", then the converter should output $H = 0100_2$. Assume that the inputs are always legal hexadecimal scancodes.

Use the **when** statement syntax to describe the output in terms of the input.

Homework 2 – Homework

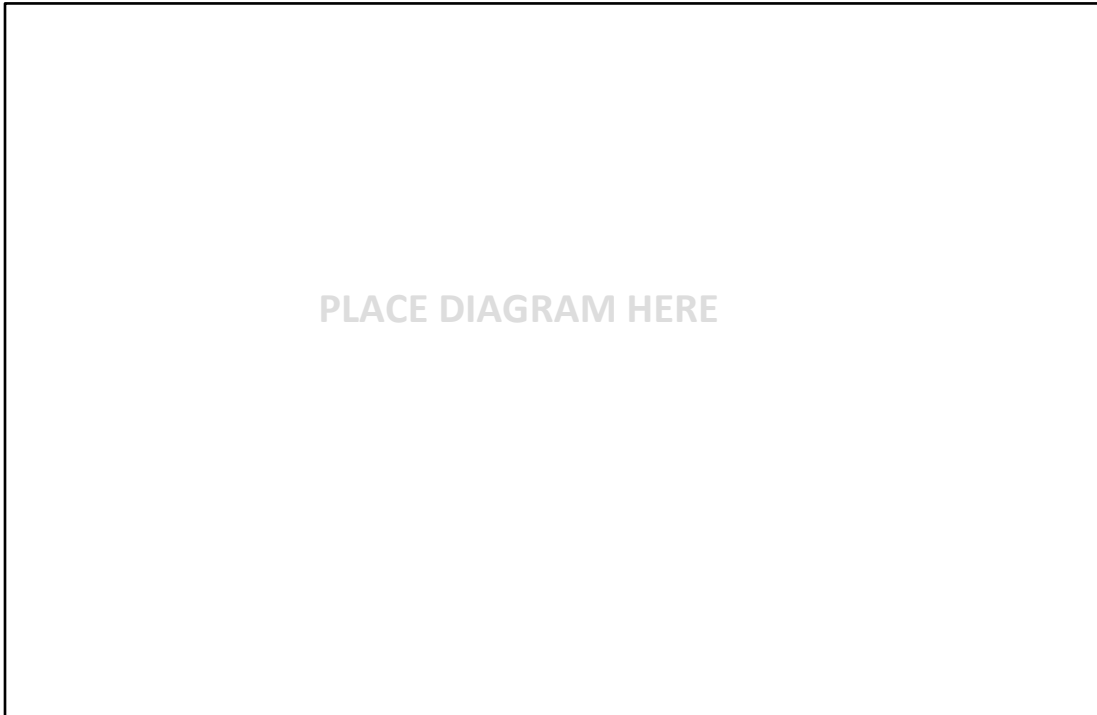- a. Create a testbench to simulate and demonstrate your function works for all 10 values in the first table. Provide a cropped screenshot of the resulting simulation timing diagram below - make the signal values legible.



- b. In Github, provide the VHDL code for your **Scancode decoder** component and testbench.